

EE6303: ELECTRIC MACHINES II
ASSIGNMENT 01

NAME : WEERAWANNI W.M.C.R.

REG No. : EG/ 2019/ 3774

SEMESTER: 06

DATE : 08 /07 /2023

1. An ideal 3-phase step-down transformer connected delta/star delivers power to a balanced 3-phase load of 120 kVA at 0.8 power factor. The input line voltage is 11 kV and the turn ratio of the transformer, phase-to-phase is 10. Determine the line voltages, line currents, phase voltages and phase currents on both the primary and the secondary sides.

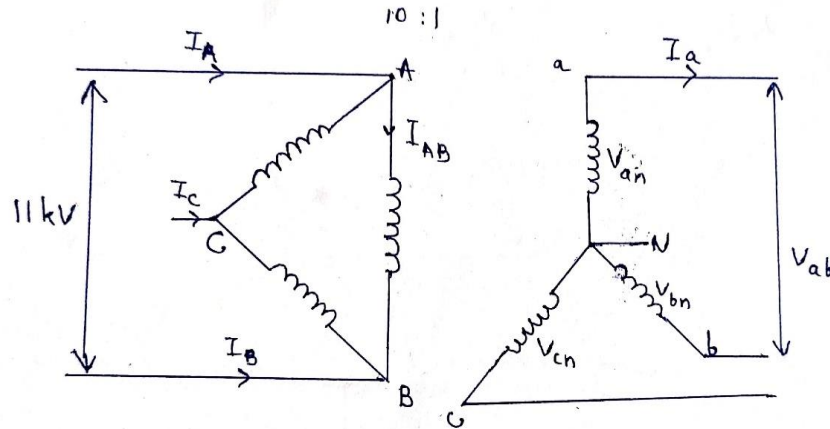


Figure 1: Ideal 3-phase step down transformer connected in delta/star

Output power to the load	= 120 KVA
Input Line voltage	= Phase Voltage
	= 11 kV
Power factor	= 0.8
Phase to phase turn ration	= 10

Considering phase voltages of primary and secondary side,

$$\frac{V_{AB}}{V_{an}} = \frac{V_{BC}}{V_{bn}} = \frac{V_{CA}}{V_{cn}} = 10$$

Since primary side is delta connected,

Primary side line voltage = Primary side phase voltage

$$v_{AB} = 11 \angle 0^\circ \text{ kV}$$

$$v_{BC} = 11 \angle -120^\circ \text{ kV}$$

$$v_{CA} = 11 \angle -240^\circ \text{ kV}$$

Secondary side phase voltages,

$$|v_{an}| = \frac{V_{AB}}{10}$$

$$|v_{an}| = \frac{11 \times 10^3}{10}$$

$$|v_{an}| = 1.1 \times 10^3$$

$$\underline{\underline{|v_{an}| = 1.1 \text{ kV}}}$$

$$v_{an} = 1.1 \angle 0^\circ \text{ kV}$$

$$v_{bn} = 1.1 \angle -120^\circ \text{ kV}$$

$$v_{cn} = 1.1 \angle -240^\circ \text{ kV}$$

Secondary side line to line voltage,

$$|v_{ab}| = \sqrt{3} \times 1.1 \times 10^3$$

$$\underline{\underline{|v_{ab}| = 1.905 \text{ kV}}}$$

$$v_{ab} = 1.905 \angle 30^\circ \text{ kV}$$

$$v_{bc} = 1.905 \angle -90^\circ \text{ kV}$$

$$v_{ca} = 1.905 \angle -210^\circ \text{ kV}$$

Considering primary side,

$$S = \sqrt{3} v_{AB} I_A$$

$$120 \times 10^3 = \sqrt{3} \times 11 \times 10^3 \times |I_A|$$

$$\underline{\underline{|I_A| = 6.298 \text{ A}}}$$

Therefore,

Primary side line currents,

$$I_A = 6.298 \angle -66.87^\circ \text{ A}$$

$$I_B = 6.298 \angle -186.87^\circ \text{ A}$$

$$I_C = 6.298 \angle -306.87^\circ \text{ A}$$

Primary side phase current, I_{AB}

$$|I_{AB}| = \frac{6.298}{\sqrt{3}} A$$

$$\underline{\underline{|I_{AB}| = 3.636 A}}$$

$$I_{AB} = 3.636 \angle -36.87^\circ A$$

$$I_{BC} = 3.636 \angle -156.87^\circ A$$

$$I_{CA} = 3.636 \angle -276.87^\circ A$$

Now,

$$\frac{I_{AB}}{I_a} = \frac{I_{BC}}{I_b} = \frac{V_{CA}}{I_c} = \frac{1}{10}$$

Therefore,

$$\begin{aligned} \text{Secondary side phase current} &= 10 \times |I_{AB}| \\ &= 10 \times 3.636 A \\ &= \underline{\underline{36.36 A}} \end{aligned}$$

Secondary side Line current = Secondary side phase current

$$\underline{\underline{|I_a| = 36.36 A}}$$

$$I_a = 36.36 \angle -36.87^\circ A$$

$$I_b = 36.36 \angle -156.87^\circ A$$

$$I_c = 36.36 \angle -276.87^\circ A$$

2. Two single-phase transformers operate in parallel to supply a load of $44 + j 18.6 \Omega$. The transformer A has a secondary emf of 600 V on open circuit with an internal impedance of $1.8 + j 5.6 \Omega$ referred to the secondary. The corresponding figures for transformer B are 610 V and $1.8 + j 7.4 \Omega$. Calculate the terminal voltage, current and power factor of each transformer.

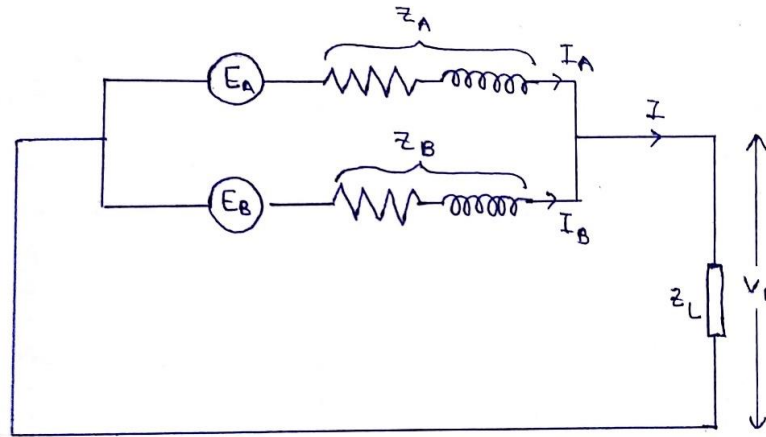


Figure 2: Single phase transformers operate in parallel to supply a load

$$\begin{aligned}\text{Load} &= (44 + j18.6) \Omega \\ &= 47.770 \angle 22.92^\circ \Omega\end{aligned}$$

Transformers data referred to secondary side,

$$\begin{aligned}\text{A: Secondary emf } (E_A) &= 600\text{V} \\ \text{Internal Impedance } (Z_A) &= 1.8 + j5.6 \\ &= 5.882 \angle 72.18^\circ \Omega\end{aligned}$$

$$\begin{aligned}\text{B: Secondary emf } (E_B) &= 610\text{V} \\ \text{Internal Impedance } (Z_B) &= 1.8 + j7.4 \\ &= 7.616 \angle 76.33^\circ \Omega\end{aligned}$$

According to the Figure 2,

$$I_A + I_B = I \quad \text{—————(01)}$$

$$I_A = \frac{E_A - V_L}{Z_A}$$

$$I_A = \frac{E_A - IZ_L}{Z_A} \text{ ————— (02)}$$

Similarly,

$$I_B = \frac{E_B - IZ_L}{Z_B} \text{ ————— (03)}$$

From Equation (01), (02) and (03),

$$I_A = \frac{E_A Z_B + (E_A - E_B) Z_L}{Z_A Z_B + Z_L (Z_A + Z_B)} \text{ ————— (04)}$$

$$I_A = \frac{E_B Z_A + (E_B - E_A) Z_L}{Z_A Z_B + Z_L (Z_A + Z_B)} \text{ ————— (05)}$$

By using equation (04),

$$I_A = \frac{600(7.616\angle 76.33^\circ) + (600 - 610)(47.770\angle 22.92^\circ)}{(5.882\angle 72.18^\circ)(7.616\angle 76.33^\circ) + (47.770\angle 22.92^\circ)[(5.882\angle 72.18^\circ) + (7.616\angle 76.33^\circ\text{C})]}$$

$$\underline{\underline{I_A = 6.388\angle -18.96^\circ A}}$$

By using equation (05),

$$I_B = \frac{610(5.882\angle 72.18^\circ) + (610 - 600)(47.770\angle 22.92^\circ)}{(5.882\angle 72.18^\circ)(7.616\angle 76.33^\circ) + (47.770\angle 22.92^\circ)[(5.882\angle 72.18^\circ) + (7.616\angle 76.33^\circ\text{C})]}$$

$$\underline{\underline{I_B = 5.815\angle -33.53^\circ A}}$$

From Equation (01)

$$I = I_A + I_B$$

$$I = (6.388\angle -18.96^\circ) + (5.815\angle -33.53^\circ)$$

$$\underline{\underline{I = 12.105\angle -25.90^\circ}}$$

Now terminal voltage, V_L

$$V_L = IZ_L$$

$$= (12.105\angle -25.90^\circ)(47.770\angle 22.92^\circ)$$

$$\underline{\underline{V_L = 578.256\angle -2.19^\circ V}}$$

Consider transformer A,

$$\cos\phi_A = \cos(\phi_V - \phi_{I_A})$$

$$= \cos(-2.19 + 18.96)$$

$$\underline{\underline{\cos\phi_A = 0.9574 \text{ lagging}}}$$

Hence power factor of transformer A = 0.9574 lagging

Consider transformer B,

$$\cos\phi_A = \cos(\phi_V - \phi_{I_A})$$

$$= \cos(-2.19 + 33.53)$$

$$\underline{\underline{\cos\phi_A = 0.8541 \text{ lagging}}}$$

Hence power factor of transformer B = 0.8541 lagging

3. A 400/100 V, 10 kVA, 2-winding transformer is to be employed as an autotransformer to supply a 400 V circuit from a 500 V source. When tested as a 2-winding transformer at rated load, 0.85 pf lagging, its efficiency is 97%.
- Determine its kVA rating as an autotransformer.
 - Find its efficiency as an autotransformer.

(a)

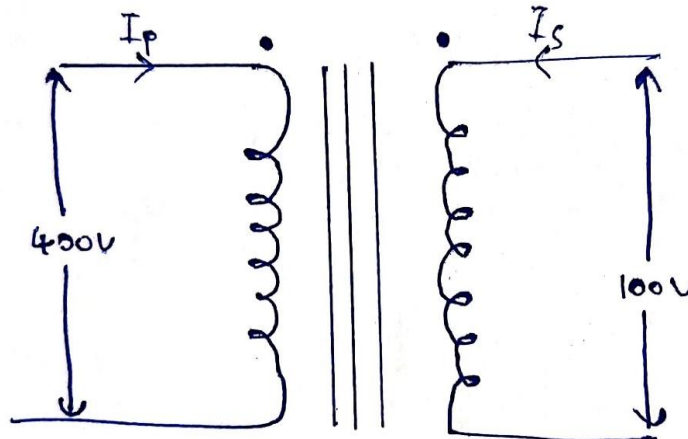


Figure 3: Two winding transformer

Considering rated conditions,

$$P = VI$$

$$I_{p, \text{rated}} = \frac{P}{V_{p, \text{rated}}}$$

$$I_{p, \text{rated}} = \frac{10 \times 10^3}{400}$$

$$I_{p, \text{rated}} = 25 \text{ A}$$

$$I_{s, \text{rated}} = \frac{P}{V_{s, \text{rated}}}$$

$$I_{s, \text{rated}} = \frac{10 \times 10^3}{100}$$

$$I_{s, \text{rated}} = 100 \text{ A}$$

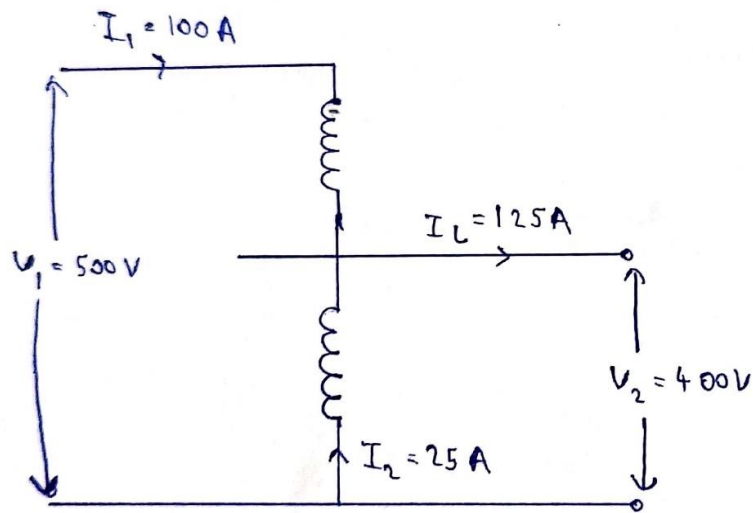


Figure 4: 2 winding transformer connected as a autotransformer

Voltage ratings of the autotransformer is,

$$S = S_{ind} + S_{cond} \text{ ————— (01)}$$

$$\begin{aligned} S_{ind} &= I_2 V_2 \\ &= 25 \text{ A} \times 400 \text{ V} \\ S_{ind} &= 10 \text{ kVA} \end{aligned}$$

$$\begin{aligned} S_{cond} &= I_1 V_2 \\ &= 100 \text{ A} \times 400 \text{ V} \\ S_{ind} &= 40 \text{ kVA} \end{aligned}$$

Therefore, rated kVA from equation 1,

$$\begin{aligned} S &= (10 + 40) \text{ kVA} \\ S &= \underline{\underline{50 \text{ kVA}}} \end{aligned}$$

(b)

Consider two winding transformers,

$$\begin{aligned}P_{out} &= S \times PF \\&= 10 \times 10^3 \times 0.85\end{aligned}$$

$$P_{out} = 8.5 \text{ kW}$$

$$\begin{aligned}P_{in} &= P_{out} + P_{loss} \\&= 8.5 \text{ kW} + P_{loss}\end{aligned}$$

$$\begin{aligned}\text{Efficiency, } \eta &= \frac{P_{out}}{P_{in}} \\0.97 &= \frac{8.5}{8.5 + P_{loss}} \\P_{loss} &= 0.263 \text{ kW}\end{aligned}$$

Considering Autotransformer,

$$\begin{aligned}P_{out} &= 50 \times 10^3 \times 0.85 \\&= 42.5 \text{ kW}\end{aligned}$$

$$\begin{aligned}\eta &= \frac{42.5}{42.5 + 0.263} \times 100\% \\&= \underline{\underline{99.385\%}}\end{aligned}$$

Therefore, Auto transformer efficiency is 99.385%

4. A 6000 V/150 V, 50 Hz potential transformer has the following parameters with reference to Figure Q4 as seen from HV side.

$$X_1 = 876 \, \Omega$$


$$X'_2 = 996 \, \Omega$$

$$X_m = 398 \, \text{k}\Omega$$

$$R_1 = 684 \, \Omega$$

$$R'_2 = 887 \, \Omega$$

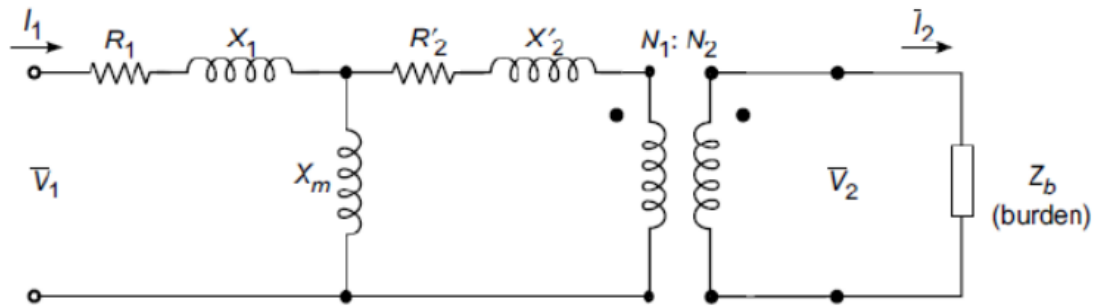- (a) The primary is excited at 6400 V and the secondary is left open. Calculate the secondary voltage magnitude and phase.
- b) The secondary is loaded with 10 k Ω resistance, repeat part a).
- c) Calculate the percentage error in the measurement for the two cases in part a) and b)



a)

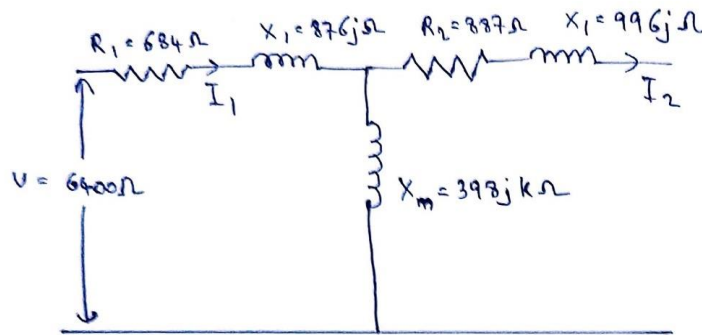


Figure 6: Equivalent circuit of a potential transformer when left open

Secondary side is open. Therefore, $I_2 = 0$.

Hence,

$$\begin{aligned} I_1 &= \frac{6400}{684 + 876j + 398000j} \\ &= 2.751 \times 10^{-5} - 0.016j \\ I_1 &= 0.016 \angle -89.902^\circ \text{ A} \end{aligned}$$

Secondary voltage referred to primary,

$$\begin{aligned} V_2' &= I_1 X_m \\ &= (0.016 \angle -89.902^\circ) \times 398000j \\ V_2' &= 6385.935 \angle 0.098^\circ \text{ V} \end{aligned}$$


Turn ratio,

$$\begin{aligned} \frac{N_1}{N_2} &= \frac{V_p}{V_s} = a \\ a &= \frac{6000}{150} \\ a &= 40 \end{aligned}$$

Secondary voltage, V_2

$$\begin{aligned} V_2 &= \frac{V_2'}{40} \\ &= \frac{6385.935 \angle 0.098^\circ}{40} \\ V_2 &= \underline{\underline{159.648 \angle 0.098^\circ \text{ V}}} \end{aligned}$$

b)

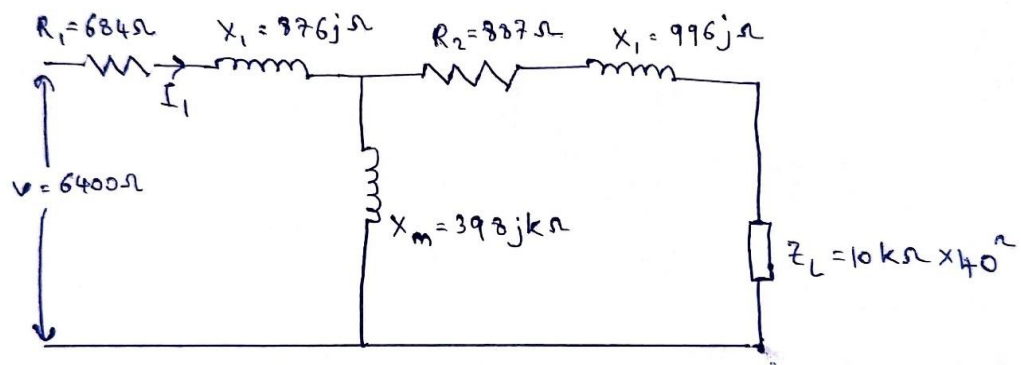

$$\begin{aligned} Z_L' &= 10 \times 10^3 \times 40^2 \\ &= 16 \times 10^6 \Omega \end{aligned}$$

$$\begin{aligned} Z_{eq} &= 684 + 876j + (398000j) // (887 + 996j + 16 \times 10^6) \\ &= 398.770 \angle 88.48^\circ \text{ k}\Omega \end{aligned}$$

Therefore,

$$I_1 = \frac{6400}{(398.770 \times 10^3 \angle 88.48^\circ)}$$

$$= 0.016 \angle -88.48^\circ \text{ A}$$

Now,

$$I_2 = \frac{398000j}{398000j + 887 + 996j + 16 \times 10^6} \times 0.016 \angle -88.48^\circ \text{ A}$$

$$= 3.979 \times 10^{-4} \angle 0.092^\circ \text{ A}$$

Therefore, secondary voltage referred to primary, V_2'

$$V_2' = I_2 Z_L'$$

$$= (3.979 \times 10^{-4} \angle 0.092^\circ) \times 16 \times 10^6$$

$$V_2' = 6366.4 \angle 0.092^\circ \text{ V}$$

Secondary voltage, V_2

$$V_2 = \frac{6366.4 \angle 0.092^\circ}{40^2}$$

$$\underline{\underline{V_2 = 159.16 \angle 0.092^\circ \text{ V}}}$$

c) The actual value should be $= \frac{6400}{6000} \times 150$

$$= 160 \text{ V}$$

For part a),

$$\text{Percentage error} = \frac{|159.648 - 160|}{160} \times 100\%$$

$$\underline{\underline{\text{Percentage error} = 0.22\%}}$$

For part b),

$$\text{Percentage error} = \frac{|159.160 - 160|}{160} \times 100\%$$

$$\underline{\underline{\text{Percentage error} = 0.525\%}}$$